

MCT
 MANJARA CHARITABLE TRUST
RAJIV GANDHI INSTITUTE OF TECHNOLOGY, MUMBAI
 Department of Applied Sciences & Humanities

INTERNAL ASSESMENT BEEE (IA) - I

Date: - 23/10/2024

Max. Marks: 20

Duration: 1 hrs



Class: FE

Name of the Course: Basic Electrical and Electronics Engineering

Branch: All


Instructions:

1. Question 1 is compulsory for 10 Marks (5 questions of 2 marks)
2. From Question 2 (Solve any one)
3. From Question 3 (Solve any one)
4. Figures to the right of the question indicate full marks.
5. Assume the suitable data wherever necessary.
6. Illustrate your answers using neat diagrams wherever necessary.

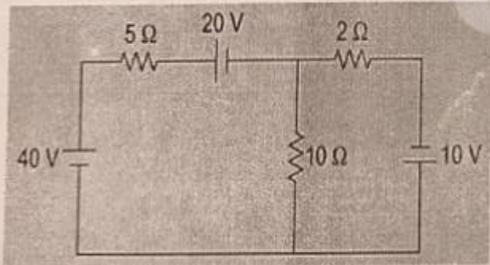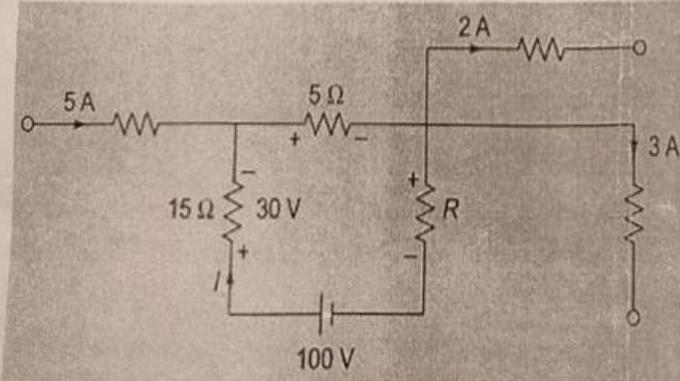Questions	Maximum Marks	Bloom's Taxonomy Level	Course Outcomes
<p>Q1. i. Calculate the value of V_{TH} when current flowing through 2Ω by Thevenin's theorem.</p> 	2	3	CO1
<p>Q1. ii. The voltage drop across the 15Ω resistor is 30V, having the polarity indicated. Compute the value of R</p> 	2	3	CO1

Q1. iii. What is superposition theorem? Explain.	2	2	CO1
Q1. iv. What is Zener diode? Draw the forward biased characteristics of zener diode.	2	1	CO5
Q1.v. What is BJT? Draw the common emitter (CE) configuration diagram	2	1	CO6

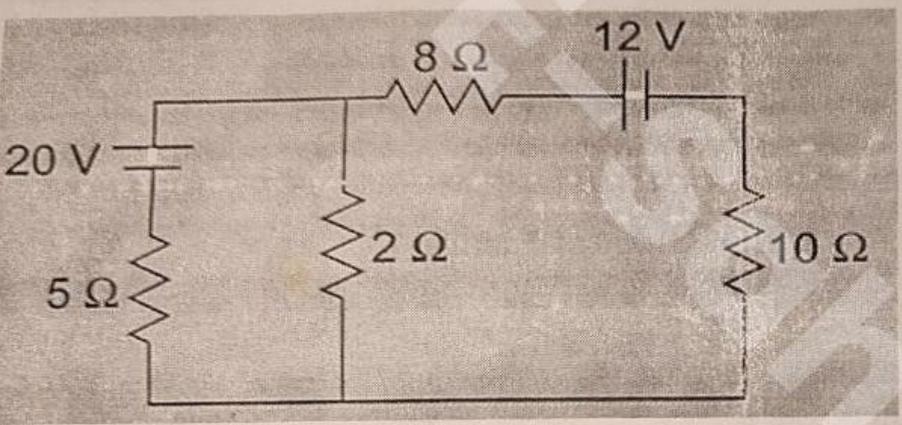Q2. a Calculate the value of current flowing through 10Ω resistor using Norton theorem.



5	3	CO1
---	---	-----

OR

Q2. B Discuss in detail delta to star transformation method.	5	2	CO1
--	---	---	-----

Q3. A Draw and explain the structure and operation of LED in detail.	5	2	CO5
--	---	---	-----

OR

Q3. B. Draw and discuss the construction and operation of n-channel FET.	5	2	CO6
--	---	---	-----